

Total Pages : 4

KN-263

BCA (Part-I) Examination, 2022

**THEORETICAL FOUNDATION OF
COMPUTER SCIENCE**

(Introductory Electronics)

[Paper : Third]

Time Allowed : Three Hours

Maximum Marks : 50

Minimum Passing Marks : 17

Note : Attempt all the **five** questions. **One** question from each unit is **compulsory**. All questions carry equal marks.

Unit-I

1. What are Transistors? Describe working process of CE amplifier.

OR

KN-263/1000

(1)

[P.T.O.]

Explain the following :

- (a) RTL
- (b) DTL
- (c) TTL

Unit-II

2. Explain the steps to construct a resistor in a monolithic IC.

OR

Briefly explain P-Substrate with suitable diagram.

Unit-III

3. Evaluate the following :

- (a) $(1011011)_2 - (10010)_2$
- (b) $(FA7C)_{16} = (?)_8$

OR

Explain 1's and 2's complement with suitable example.

Unit-IV

4. What are the universal gates? Explain with suitable diagram.

OR

Explain the Karnaugh map with its types.

Unit-V

5. Draw and explain JK Flip-Flop with suitable diagram.

OR

What is a multiplexer? Draw and explain 4×1 MUX.

---X---